

# AN2867 Application note

# Oscillator design guide for STM8AF/AL/S, STM32 MCUs and MPUs

#### Introduction

Many designers know oscillators based on Pierce-Gate topology (Pierce oscillators), but not all of them really understand how they operate, and only a few master their design. In practice, limited attention is paid to the oscillator design, until it is found that it does not operate properly (usually when the final product is already in production). A crystal not working as intended results in project delays, if not overall failure.

The oscillator must get the proper amount of attention during the design phase, well before moving to manufacturing, to avoid the nightmare scenario of products failing in application.

This document introduces the Pierce oscillator basics, and provides guidelines for its design. It also shows how to determine the external components, and provides guidelines for correct PCB design and for selecting crystals and external components.

To speed up the application development, the recommended crystals (HSE and LSE) for the products listed in *Table 1* are detailed in *Section 5: Recommended resonators for STM32 MCUs/MPUs* and *Section 6: Recommended crystals for STM8AF/AL/S microcontrollers*.

Table 1. Applicable products

Туре	Product categories
	STM8S Series, STM8AF Series and STM8AL Series
	STM32 32-bit Arm <sup>®</sup> Cortex <sup>®</sup> MCUs
Microcontrollers	STM32 Wireless MCUs
	STM32 Ultra Low Power MCUs
	STM32 High Performance MCUs
Microprocessors	STM32 Arm® Cortex® MPUs

August 2022 AN2867 Rev 16 1/59

Contents AN2867

## **Contents**

2.1 Negative resistance 2.2 Transconductance 2.3 Negative-resistance oscillator principles  3 Pierce oscillator design 3.1 Introduction to Pierce oscillators 3.2 Feedback resistor 3.3 Load capacitance 3.4 Oscillator transconductance 3.5 Drive level and external resistor calculation 3.5.1 Calculating the drive level 3.5.2 Another drive level measurement method 3.5.3 Calculating the external resistor 3.6 Start-up time 3.7 Crystal pullability 3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components 4.1 Low-speed oscillators embedded in STM32 MCUs / MPUs	6
2.2 Transconductance 2.3 Negative-resistance oscillator principles  3 Pierce oscillator design 3.1 Introduction to Pierce oscillators 3.2 Feedback resistor 3.3 Load capacitance 3.4 Oscillator transconductance 3.5 Drive level and external resistor calculation 3.5.1 Calculating the drive level 3.5.2 Another drive level measurement method 3.5.3 Calculating the external resistor 3.6 Start-up time 3.7 Crystal pullability 3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	8
2.3 Negative-resistance oscillator principles  Pierce oscillator design 3.1 Introduction to Pierce oscillators 3.2 Feedback resistor 3.3 Load capacitance 3.4 Oscillator transconductance 3.5 Drive level and external resistor calculation 3.5.1 Calculating the drive level 3.5.2 Another drive level measurement method 3.5.3 Calculating the external resistor 3.6 Start-up time 3.7 Crystal pullability 3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	8
3.1 Introduction to Pierce oscillators 3.2 Feedback resistor 3.3 Load capacitance 3.4 Oscillator transconductance 3.5 Drive level and external resistor calculation 3.5.1 Calculating the drive level 3.5.2 Another drive level measurement method 3.5.3 Calculating the external resistor 3.6 Start-up time 3.7 Crystal pullability 3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	9
3.1 Introduction to Pierce oscillators 3.2 Feedback resistor 3.3 Load capacitance 3.4 Oscillator transconductance 3.5 Drive level and external resistor calculation 3.5.1 Calculating the drive level 3.5.2 Another drive level measurement method 3.5.3 Calculating the external resistor 3.6 Start-up time 3.7 Crystal pullability 3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	10
3.2 Feedback resistor 3.3 Load capacitance 3.4 Oscillator transconductance 3.5 Drive level and external resistor calculation 3.5.1 Calculating the drive level 3.5.2 Another drive level measurement method 3.5.3 Calculating the external resistor 3.6 Start-up time 3.7 Crystal pullability 3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	11
3.3 Load capacitance 3.4 Oscillator transconductance 3.5 Drive level and external resistor calculation 3.5.1 Calculating the drive level 3.5.2 Another drive level measurement method 3.5.3 Calculating the external resistor 3.6 Start-up time 3.7 Crystal pullability 3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	11
3.4 Oscillator transconductance 3.5 Drive level and external resistor calculation 3.5.1 Calculating the drive level 3.5.2 Another drive level measurement method 3.5.3 Calculating the external resistor 3.6 Start-up time 3.7 Crystal pullability 3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	11
3.5 Drive level and external resistor calculation 3.5.1 Calculating the drive level 3.5.2 Another drive level measurement method 3.5.3 Calculating the external resistor 3.6 Start-up time 3.7 Crystal pullability 3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	12
3.5.1 Calculating the drive level 3.5.2 Another drive level measurement method 3.5.3 Calculating the external resistor 3.6 Start-up time 3.7 Crystal pullability 3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	13
3.5.2 Another drive level measurement method 3.5.3 Calculating the external resistor 3.6 Start-up time 3.7 Crystal pullability 3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	14
3.5.3 Calculating the external resistor  3.6 Start-up time  3.7 Crystal pullability  3.8 Safety factor  3.8.1 Definition  3.8.2 Measurement methodology  3.8.3 Safety factor for STM32 and STM8 oscillators  3.9 Oscillation modes  3.9.1 What are fundamental and overtone modes?  3.9.2 Third overtone mode: pros and cons  3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	14
3.6 Start-up time 3.7 Crystal pullability 3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	16
3.7 Crystal pullability 3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	16
3.8 Safety factor 3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	17
3.8.1 Definition 3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	17
3.8.2 Measurement methodology 3.8.3 Safety factor for STM32 and STM8 oscillators 3.9 Oscillation modes 3.9.1 What are fundamental and overtone modes? 3.9.2 Third overtone mode: pros and cons 3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	18
3.8.3 Safety factor for STM32 and STM8 oscillators  3.9 Oscillation modes  3.9.1 What are fundamental and overtone modes?  3.9.2 Third overtone mode: pros and cons  3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	18
3.9 Oscillation modes  3.9.1 What are fundamental and overtone modes?  3.9.2 Third overtone mode: pros and cons  3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	19
3.9.1 What are fundamental and overtone modes?	19
3.9.2 Third overtone mode: pros and cons	20
3.9.3 Considerations for crystals interfaced with STM32 products  4 Guidelines to select a suitable crystal and external components	20
4 Guidelines to select a suitable crystal and external components	21
and external components	22
	23
4.2 How to select an STM32-compatible crystal	
5 Recommended resonators for STM32 MCUs/MPUs	29



	5.1	STM32-compatible high-speed resonators	. 29
	5.2	STM32-compatible low-speed resonators	. 29
6	Rec	ommended crystals for STM8AF/AL/S microcontrollers	43
	6.1	Part numbers of recommended crystal oscillators	43
	6.2	Recommended ceramic resonators	. 44
7	Tips	for improving oscillator stability	45
	7.1	PCB design guidelines	45
	7.2	PCB design examples	47
	7.3	Soldering guidelines	. 51
	7.4	LSE sensitivity to PC13 activity	. 51
8	Refe	erence documents	. 53
9	FAQ	ls	. 54
10	Con	clusion	55
11	Revi	ision history	56

Contents

List of tables AN2867

# List of tables

Table 1.	Applicable products	1
Table 2.	Example of equivalent circuit parameters	7
Table 3.	Typical feedback resistor values for given frequencies	12
Table 4.	Safety factor (Sf) for STM32 and STM8 oscillators	19
Table 5.	LSE oscillators embedded into STM32 MCUs/MPUs	25
Table 6.	HSE oscillators embedded in STM32 MCUs/MPUs	29
Table 7.	Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products	30
Table 8.	KYOCERA compatible crystals (not exhaustive list)	43
Table 9.	NDK compatible crystals (not exhaustive list)	
Table 10.	Recommended conditions (for consumer)	
Table 11.	Recommended conditions (for CAN-BUS)	
Table 12	Document revision history	56

AN2867 List of figures

# List of figures

Figure 1.	Quartz crystal model	. 6
Figure 2.	Impedance in the frequency domain	
Figure 3.	I-V curve of a dipole showing a negative trans-resistance area	. 9
Figure 4.	Block diagram of a typical oscillation loop based on a crystal resonator	10
Figure 5.	Pierce oscillator circuitry	11
Figure 6.	Inverter transfer function	12
Figure 7.	Current drive measurement with a current probe	15
Figure 8.	Negative resistance measurement methodology description	19
Figure 9.	Fundamental and overtone frequencies of an AT-cut quartz crystal	20
Figure 10.	Quartz crystal theoretical model with third overtone	21
Figure 11.	Oscillator implementation for third overtone	21
Figure 12.	Classification of low-speed crystal resonators	23
Figure 13.	Recommended layout for an oscillator circuit	46
Figure 14.	PCB with separated GND plane and guard ring around the oscillator	47
Figure 15.	GND plane	47
Figure 16.	Signals around the oscillator	47
Figure 17.	Preliminary design (PCB design guidelines not respected)	
Figure 18.	Final design (following guidelines)	49
Figure 19.	GND plane	49
Figure 20.	Top layer view	
Figure 21.	PCB guidelines not respected	
Figure 22.	PCB guidelines respected	51




AN2867 Rev 16 5/59

## 1 Quartz crystal properties and model

A quartz crystal is a piezoelectric device converting electric energy into mechanical energy and vice versa. The transformation occurs at the resonant frequency. The quartz crystal can be modeled as shown in *Figure 1*.

Figure 1. Quartz crystal model

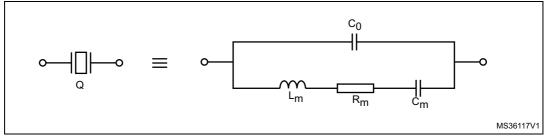


- C<sub>0</sub>: represents the shunt capacitance resulting from the capacitor formed by the electrodes
- L<sub>m</sub> (motional inductance): represents the vibrating mass of the crystal
- C<sub>m</sub> (motional capacitance): represents the elasticity of the crystal
- R<sub>m</sub> (motional resistance): represents the circuit losses

The impedance of the crystal (assuming that  $R_{\text{m}}$  is negligible) is

$$Z = \frac{j}{w} \times \frac{w^2 \times L_m \times C_m - 1}{(C_0 + C_m) - w^2 \times L_m \times C_m \times C_0}$$

Figure 2 shows the impedance in the frequency domain.

Figure 2. Impedance in the frequency domain

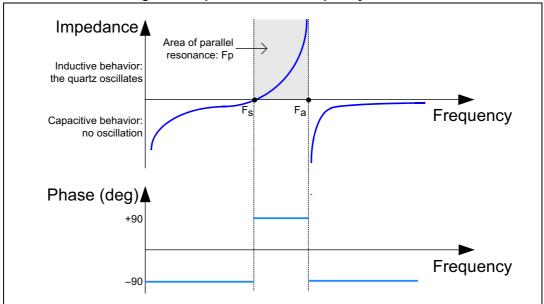

 $F_s$  is the series resonant frequency when Z = 0. Its expression can be deduced from equation (1) as follows:

$$F_{S} = \frac{1}{2\pi \sqrt{L_{m}C_{m}}}$$

F<sub>a</sub> is the antiresonant frequency when Z tends to infinity. Using equation (1), it is expressed as follows:

$$F_{a} = F_{s} \sqrt{1 + \frac{C_{m}}{C_{0}}}$$

The region delimited by  $F_s$  and  $F_a$  (shaded area in *Figure 2*) is the area of parallel resonance. In this region, the crystal operates in parallel resonance and behaves as an inductance that adds an additional 180° phase to the loop. Its frequency  $F_p$  (or  $F_L$ : load frequency) has the following expression:

(4) 
$$F_{p} = F_{s} \left( 1 + \frac{C_{m}}{2(C_{0} + C_{1})} \right)$$

According to this equation, the oscillation frequency of the crystal can be tuned by varying the load capacitance  $C_L$ . This is why, in their datasheets, crystal manufacturers indicate the exact  $C_L$  required to make the crystal oscillate at the nominal frequency.

*Table 2* gives an example of equivalent crystal circuit component values for an 8 MHz nominal frequency.

Equivalent component	Value
R <sub>m</sub>	8 Ω
L <sub>m</sub>	14.7 mH
C <sub>m</sub>	0.027 pF
C <sub>0</sub>	5.57 pF

Table 2. Example of equivalent circuit parameters

Using equations (2), (3) and (4) it is possible to determine  $F_s$ ,  $F_a$ , and  $F_p$  of this crystal:

- $F_s = 7988768 \text{ Hz}$
- F<sub>a</sub> = 8008102 Hz

If the load capacitance  $C_L$  is equal to 10 pF, the crystal oscillates at  $F_p$  = 7995695 Hz.

To have an oscillation frequency of exactly 8 MHz, C<sub>L</sub> must be 4.02 pF.

57

AN2867 Rev 16 7/59

Oscillator theory AN2867

## 2 Oscillator theory

Oscillators are among the backbone components of modern digital ICs. They can be classified into different subfamilies, depending upon their topology and operating principles. For each subfamily there is a mathematical model that can be used to study the oscillator behavior, and theoretically determine its performance.

This section deals only with harmonic oscillators (relaxation oscillators are out of the scope of this document), with particular focus (see *Section 3*) on Pierce oscillators. This is because all the oscillators requiring external passive components (resonator, load capacitors, etc.) covered by this document are of the previously mentioned type and topology.

The harmonic oscillator family can be divided into two main subfamilies:

- negative-resistance oscillators
- positive-feedback oscillators.

These two subfamilies of oscillators are similar for what concerns the output waveform. They deliver an oscillating waveform at the desired frequency. This waveform is typically composed of a fundamental sine wave of the desired frequency, plus a sum of overtone harmonics (at frequencies multiple of the fundamental one), due to the nonlinearity of components of the oscillation loop.

The two subfamilies differ in their operating principles, a specific mathematical model describes and analyzes each of them.

Positive-feedback oscillators are usually modeled using the Barkhausen model, where an oscillator must fulfill the Barkhausen criterion to maintain a stable oscillation at the desired frequency.

The Barkhausen model is not fully adequate to describe negative-resistance oscillators: the most suitable approach is to use the negative-resistance model described in [1].

STM32 microcontrollers and microprocessors (based on Arm<sup>®(a)</sup> cores) feature low-speed external (LSE) and high-speed external (HSE) oscillators designed according to the negative-resistance principle, hence this section focuses on the presentation of this model.

## 2.1 Negative resistance

Theoretically speaking, a negative resistance is a dipole that absorbs heat and converts the energy into an electrical current, proportional to the applied voltage, but flowing in the opposite direction (the opposite mechanism of an electrical resistance). In the real world, such a dipole does not exist.

arm

a. Arm is a registered trademark of Arm Limited (or its subsidiaries) in the US and/or elsewhere.

AN2867 Oscillator theory

The term "negative resistance" is actually a misnomer of the "negative trans-resistance", defined by the ratio between a given voltage variation ( $\Delta V$ ) and the induced current variation ( $\Delta I$ ). Unlike the resistance, always positive, the trans-resistance (also known as differential resistance) can be either positive or negative. *Figure 3* gives the current-voltage curve for a dipole that shows a negative trans-resistance region. It is obvious that the V/I ratio is always positive, this is not the case for the  $\Delta V$  /  $\Delta I$  ratio.

The portion of the I-V curve in purple shows a negative trans-resistance:

$$\frac{\Delta V}{\Delta I} = \frac{V(D) - V(C)}{I(D) - I(C)} < 0$$

The portions in blue feature a positive trans-resistance:

$$\frac{\Delta V}{\Delta I} = \frac{V(B) - V(A)}{I(B) - I(A)} > 0$$

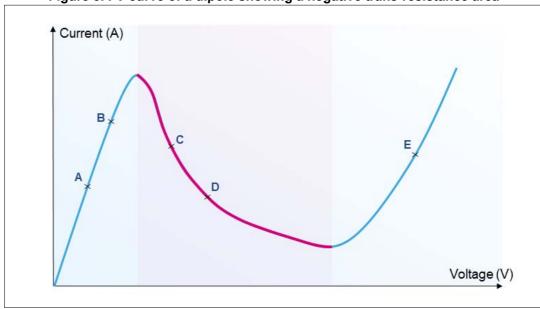


Figure 3. I-V curve of a dipole showing a negative trans-resistance area

#### 2.2 Transconductance

Similarly to the conductance, defined as the inverse of the resistance, the transconductance is defined as the inverse of the trans-resistance. Transconductance can also be defined as the differential conductance, expressed as  $\Delta I/\Delta V$ .

Oscillator theory AN2867

### 2.3 Negative-resistance oscillator principles

An oscillation loop is made of two branches (see Figure 4):

The active branch, composed by the oscillator itself, provides the energy to make the
oscillation start and build up until it reaches a stable phase. When a stable oscillation is
reached, this branch provides the energy to compensate for the losses of the passive
branch.

• The passive branch is mainly composed by the resonator, the two load capacitors and all the parasitic capacitances.

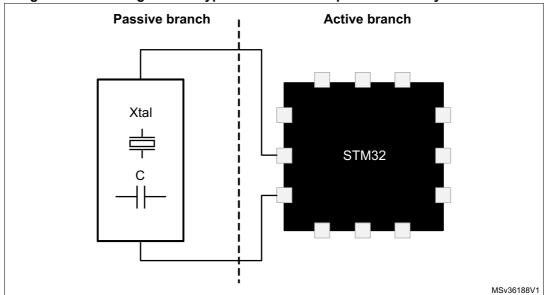


Figure 4. Block diagram of a typical oscillation loop based on a crystal resonator

According to the small signals theory, and when the active branch (oscillator part) is correctly biased, to maintain a stable oscillation around the oscillator biasing voltage the latter must have its transconductance equal to the passive branch conductance.

However, at start-up, the oscillator transconductance must be higher than (multiple of) the conductance of the passive part of the oscillation loop, to maximize the possibility to build up the oscillation from the inherent noise of the oscillation loop. Note that an excessive oscillator transconductance compared to the oscillation loop passive branch conductance can saturate the oscillation loop and cause a start-up failure.

To ensure the oscillator ability to start successfully, and to maintain stable oscillation, a ratio between the negative resistance of the oscillation loop and the crystal maximal equivalent series resistance (ESR) is specified for STM32 and STM8 products. It is recommended to have a ratio higher than 5 for the HSE oscillators, and higher than 3 for the LSE oscillators.

## 3 Pierce oscillator design

This section describes the different parameters, and how to determine their values in order to be compliant with the Pierce oscillator design.

#### 3.1 Introduction to Pierce oscillators

Pierce oscillators are variants of Colpitts oscillators, widely used with crystal resonators. A Pierce oscillator (see *Figure 5*) requires a reduced set of external components, this results in a lower final design cost. In addition, the Pierce oscillator is known for its stable oscillation frequency when paired with a crystal resonator, in particular a quartz-crystal resonator.

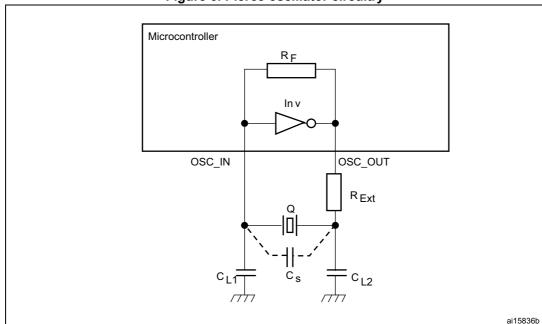


Figure 5. Pierce oscillator circuitry

- Inv: the internal inverter that works as an amplifier
- Q: crystal quartz or a ceramic resonator
- R<sub>F</sub>: internal feedback resistor
- R<sub>Fxt</sub>: external resistor to limit the inverter output current
- C<sub>L1</sub> and C<sub>L2</sub>: are the two external load capacitances
- C<sub>s</sub>: stray capacitance, is the sum of the device pin capacitance (OSC\_IN and OSC\_OUT) and the PCB (a parasitic) capacitance.

#### 3.2 Feedback resistor

In most STMicroelectronics MCUs/MPUs,  $R_F$  is embedded in the oscillator circuitry. Its role is to make the inverter act as an amplifier. The feedback resistor is connected between  $V_{in}$  and  $V_{out}$  to bias the amplifier at  $V_{out} = V_{in}$ , and force it to operate in the linear region (shaded

47/

AN2867 Rev 16 11/59

area in *Figure 6*). The noise (for example, the thermal noise of the crystal) is amplified within the range of serial to parallel frequency  $(F_a, F_p)$ , thus starting the oscillation.

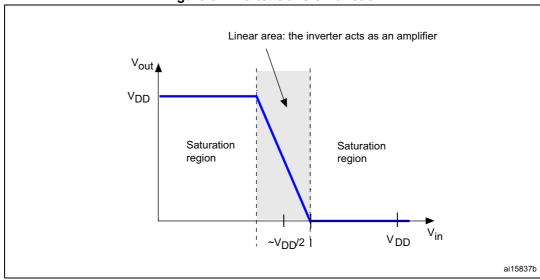


Figure 6. Inverter transfer function

Table 3 provides typical values of R<sub>F</sub>.

Table 3. Typical reedback resistor values for given frequencies								
Frequency	Feedback resistor range							
32.768 kHz	10 to 25 MΩ							
1 MHz	5 to 10 MΩ							
10 MHz	1 to 5 MΩ							
20 MHz	470 kΩ to 5 MΩ							

Table 3. Typical feedback resistor values for given frequencies

## 3.3 Load capacitance

The load capacitance is the terminal capacitance of the circuit connected to the crystal oscillator. This value is determined by the external capacitors  $C_{L1}$  and  $C_{L2}$  and the stray capacitance of the printed circuit board and connections  $(C_s).$  The  $C_L$  value is specified by the crystal manufacturer. For the frequency to be accurate, the oscillator circuit has to show the same load capacitance to the crystal as the one the crystal was adjusted for. Frequency stability requires that the load capacitance be constant. The external capacitors  $C_{L1}$  and  $C_{L2}$  are used to tune the desired value of  $C_L$  to reach the value specified by the crystal manufacturer.

The following equation gives the expression of C<sub>L</sub>:

$$C_L = \frac{C_{L1} \times C_{L2}}{C_{L1} + C_{L2}} + C_s$$

47/

For example, with  $C_L = 15 \text{ pF}$  and  $C_s = 5 \text{ pF}$ ,

$$C_L - C_s = \frac{C_{L1} \times C_{L2}}{C_{L1} + C_{L2}} = 10 \text{ pF}$$

hence  $C_{L1} = C_{L2} = 20 \text{ pF}.$ 

#### 3.4 Oscillator transconductance

Theoretically, to make the oscillation start and reach a stable phase, the oscillator must provide sufficient gain to compensate for the loop losses, and to provide the energy for the oscillation buildup. When the oscillation becomes stable, the power provided to the oscillator and the power it dissipates in the loop are equal.

Practically, because of tolerances on passive component values and their dependency upon environmental parameters (such as temperature), the ratio between oscillator gain and oscillation loop critical gain cannot just exceed 1. This would induce a too long oscillator start-up time, and even prevent the oscillator from starting up.

This section describes the two approaches that can be used to check if an STM32 oscillator can be paired with a given resonator to ensure that the oscillation is started and maintained under the specified conditions for both resonator and oscillator. The approach depends on how the oscillator parameters are specified in the device datasheet:

- If the oscillation loop maximal critical crystal transconductance parameter (G<sub>m\_crit\_max</sub>) is specified, ensure that it is greater than the oscillation loop critical gain (g<sub>mcrit</sub>, see the formula below). Note that the maximum critical crystal transconductance can be named either G<sub>m\_crit\_max</sub> or G<sub>m</sub>, depending on the STM32 product documentation.
- If the oscillator transconductance parameter (g<sub>m</sub>) is specified, make sure that the gain margin ratio (gain<sub>margin</sub>) is bigger than 5.

The gain margin ratio is determined by the formula  $gain_{margin} = g_m / g_{mcrit}$ , where

- g<sub>m</sub> is the oscillator transconductance specified in the STM32 datasheet. The HSE oscillator transconductance is in the range of a dozen of mA/V, while the LSE oscillator transconductance ranges from a few to a few dozens of µA/V, depending upon the product.
- g<sub>mcrit</sub> is defined as the minimal transconductance required to maintain a stable oscillation when it is a part of the oscillation loop for which this parameter is relevant. g<sub>mcrit</sub> is computed from oscillation loop passive components parameters.

Assuming  $C_{L1} = C_{L2}$ , and that the crystal sees the same  $C_L$  on its pads as the value given by the crystal manufacturer,  $g_{mcrit}$  is expressed as follows:

$$g_{mcrit} = 4 \times ESR \times (2\pi F)^2 \times (C_0 + C_L)^2$$

where:

- ESR is the equivalent series resistance
- C<sub>0</sub> is the crystal shunt capacitance
- C<sub>I</sub> is the crystal nominal load capacitance.
- F is the crystal nominal oscillation frequency

57

AN2867 Rev 16 13/59

For example, to design the oscillation loop for the HSE oscillator embedded in an STM32F1 microcontroller with a transconductance value  $(g_m)$  of 25 mA/V, we choose a quartz crystal from Fox, with the following characteristics:

- Frequency = 8 MHz
- $C_0 = 7 pF$
- C<sub>L</sub> = 10 pF
- ESR = 80 Ω

To check if this crystal oscillates, let us calculate g<sub>mcrit</sub>:

$$g_{mcrit} = 4 \times 80 \times (2 \times \pi \times 8 \times 10^6)^2 \times (7 \times 10^{-12} + 10 \times 10^{-12})^2 = 0.23 \text{ mA/ V}$$

Calculating the gain margin gives:

$$gain_{margin} = \frac{g_m}{g_{mcrit}} = \frac{25}{0.23} = 107$$

The gain margin is sufficient to start the oscillation and the gain<sub>margin</sub> > 5 condition is reached. The oscillator is expected to reach a stable oscillation after a typical delay specified in the datasheet.

If an insufficient gain margin is found (gain<sub>margin</sub> < 5), the oscillation can start in some conditions (achieved in laboratory) when designing and testing the final application, but this does not guarantee that the oscillation starts in operating conditions. It is highly recommended that the selected crystal has a gain margin higher than or equal to 5 (try to select a crystal with a lower ESR and/or a lower  $C_{\rm L}$ ).

As a second example illustrating the case where the maximal critical crystal transconductance is given, the HSE oscillator embedded in STM32G0 microcontrollers has  $G_m = 1.5 \text{ mA} / \text{V}$ .  $g_{mcrit}$  operated for the implemented oscillator must stay below this value. The Fox quartz crystal described above respects this condition.

The conversion between the oscillator transconductance  $(g_m)$  and the oscillation loop maximal critical transconductance  $(G_{m\ crit\ max})$  is given by  $G_{m\ crit\ max} = g_m/5$ .

Note: Before any verification, the crystal chosen must vibrate at a frequency that respects the oscillator frequency range given in the STM32 datasheet.

#### 3.5 Drive level and external resistor calculation

The drive level (DL) and external resistor value ( $R_{\text{Ext}}$ ) are closely related, and are addressed in the same section.

#### 3.5.1 Calculating the drive level

The drive level is the power dissipated in the crystal. It must be limited, otherwise the quartz crystal can fail, because of excessive mechanical vibrations. The maximum drive level is specified by the crystal manufacturer, usually in mW. Exceeding this value can lead to crystal damage, or to a shorter device lifetime.

77


The drive level is given by the formula:  $DL = ESR \times I_0^2$ , where:

• ESR is the equivalent series resistor (specified by the crystal manufacturer):

$$ESR = R_m \times \left(1 + \frac{C_0}{C_L}\right)^2$$

 I<sub>Q</sub> is the current flowing through the crystal in RMS. This current can be displayed on an oscilloscope as a sine wave. The current value can be read as the peak-to-peak value (I<sub>PP</sub>). When using a current probe (as shown in *Figure 7*), the voltage scale of an oscilloscope may be converted into 1 mA / 1 mV.

Figure 7. Current drive measurement with a current probe

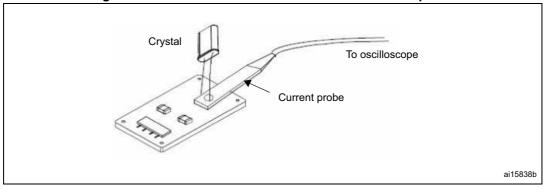

So, as described previously, when tuning the current with the potentiometer, the current through the crystal does not exceed  $I_{Qmax}$  RMS (assuming that the current through the crystal is sinusoidal).

Thus I<sub>Omax</sub> RMS is given by:

$$I_{Qmax}RMS = \sqrt{\frac{DL_{max}}{ESR}} = \frac{I_{Qmax}PP}{2\sqrt{2}}$$

Therefore, the current through the crystal (peak-to-peak value read on the oscilloscope) should not exceed a maximum peak-to-peak current ( $I_{Qmax}PP$ ) equal to:

$$I_{Qmax}PP = 2 \times \sqrt{\frac{2 \times DL_{max}}{ESR}}$$

Hence the need for an external resistor  $R_{Ext}$  (refer to *Section 3.5.3*) when  $I_Q$  exceeds  $I_{Qmax}PP$ . The addition of  $R_{Ext}$  becomes mandatory, and is added to ESR in the expression of  $I_{Qmax}$ .

4

AN2867 Rev 16 15/59

#### 3.5.2 Another drive level measurement method

The drive level can be computed as DL=  $I^2_{ORMS}$  × ESR ( $I_{ORMS}$  is the RMS AC current).

This current can be calculated by measuring the voltage swing at the amplifier input with a low-capacitance oscilloscope probe (no more than 1 pF). The amplifier input current is negligible with respect to the current through  $C_{L1}$ , so we can assume that the current through the crystal is equal to the current flowing through  $C_{L1}$ . Therefore the RMS voltage at this point is related to the RMS current by  $I_{ORMS} = 2 \, \pi \, F \, x \, V_{RMS} \, x \, C_{tot}$ , with:

- F = crystal frequency
- $V_{RMS} = \frac{V_{pp}}{2\sqrt{2}}$ , where  $V_{pp}$  is the peak-to-peak voltage measured at  $C_{L1}$  level
- $C_{tot} = C_{L1} + (C_s/2) + C_{probe}$  where:
  - C<sub>L1</sub> is the external load capacitance at the amplifier input
  - C<sub>s</sub> is the stray capacitance
  - C<sub>probe</sub> is the probe capacitance

Therefore DL = 
$$\frac{\text{ESR} \times (\pi \times \text{F} \times \text{C}_{tot})^2 \times (\text{V}_{pp})^2}{2}.$$

This value must not exceed the drive level specified by the crystal manufacturer.

Note: Use special care when measuring voltage swing at LSE input, as it is very sensitive to load capacitance. It is recommended to use a 0.1pF input capacitance probe.

#### 3.5.3 Calculating the external resistor

The role of this resistor is to limit the drive level of the crystal. With  $C_{L2}$ , it forms a low-pass filter that forces the oscillator to start at the fundamental frequency and not at overtones (prevents the oscillator from vibrating at the odd harmonics of the fundamental frequency). If the power dissipated in the crystal is higher than the value specified by the crystal manufacturer, the external resistor  $R_{\text{Ext}}$  becomes mandatory to avoid overdriving the crystal. If the power dissipated in the selected quartz is lower than the drive level specified by the crystal manufacturer, the insertion of  $R_{\text{Ext}}$  is not recommended and its value is then 0  $\Omega$ .

An initial estimation of  $R_{\text{Ext}}$  is obtained by considering the voltage divider formed by  $R_{\text{Ext}}$  and  $C_{\text{L}2}$ . Thus, the value of  $R_{\text{Ext}}$  is equal to the reactance of  $C_{\text{L}2}$ .

Therefore,  $R_{Ext}$  = 1 / (2  $\pi$  F  $C_{L2}$ ), and so, with an oscillation frequency of 8 MHz and  $C_{L2}$  = 15 pF, we have  $R_{Ext}$  = 1326  $\Omega$ .

The recommended way of optimizing  $R_{\text{Ext}}$  is to first choose  $C_{\text{L1}}$  and  $C_{\text{L2}}$  as explained before, and to connect a potentiometer in the place of  $R_{\text{Ext}}$ . The potentiometer should be initially set to be approximately equal to the capacitive reactance of  $C_{\text{L2}}$ . It should then be adjusted as required, until an acceptable output and crystal drive level are obtained.

Caution:

After calculating  $R_{\text{Ext}}$  it is recommended to recalculate the gain margin (refer to Section 3.4) to make sure that the addition of  $R_{\text{Ext}}$  has no effect on the oscillation condition. That is, the value of  $R_{\text{Ext}}$  has to be added to ESR in the expression of  $g_{\text{mcrit}}$ , and  $g_{\text{m}}$  »  $g_{\text{mcrit}}$  must also remain true:

$$g_{m} \gg g_{mcrit} = 4 \times (ESR + R_{Ext}) \times (2 \pi F)^{2} \times (C_{0} + C_{L})^{2}$$

Note:

If  $R_{Ext}$  is too low, there is a considerable decrease of the power dissipation by the crystal. If, on the other hand,  $R_{Ext}$  is too high, there is no oscillation.

### 3.6 Start-up time

This the time required by the oscillation to start and then build up until it reaches a stable oscillation phase. The start-up time depends, among other factors, on the Q-factor of the resonator used. If the oscillator is paired with a quartz-crystal resonator characterized by its high Q-factor, the start-up time is higher if a ceramic resonator is used (ceramic resonators are know for their poor Q-factor compared to quartz-crystal resonators). The start-up time also depends on the external components,  $C_{L1}$  and  $C_{L2}$ , and on the crystal frequency. The higher the crystal nominal frequency, the lower the start-up time. In addition, start-up problems are usually due to the fact that the gain margin is not properly dimensioned (as explained previously). This is caused either by  $C_{L1}$  and  $C_{L2}$  being too small or too large, or by the ESR being too high.

As an example, an oscillator paired with a few MHz nominal frequency crystal resonator typically starts up after a delay of few ms.

The start-up time of a 32.768 kHz crystal ranges from 1 to 5 s.

## 3.7 Crystal pullability

Crystal pullabilty, also known as crystal sensitivity, measures the impact of small variations of the load capacitance seen by the crystal on the oscillation frequency shifting. This parameter usually has more importance when dealing with low-speed oscillators, since they are used to clock time-keeping functions (such as real-time clock functions).

When the final application is still in design stage, the influence of this parameter on the low-speed oscillator accuracy (and consequently on all the time-keeping functions clocked by this oscillator) is not obvious. This is becauset the designer fine tunes the load capacitors until the desired oscillation frequency is obtained. When the design reaches production stage it is frozen and all the passive components including the load capacitors have their values well defined. Any change of the load capacitance induces a shift of the oscillation frequency.

Changes in the capacitive load ( $C_L$ ) seen by the crystal can be thought of as due to inadequate operation environment, and only happening when the final design is not properly operated. In practice, this is not true since changes of the load capacitance are rather frequent and must be taken into account by the designer. The main contributors to the capacitive load ( $C_L$ ) seen by the oscillator are

- the capacitance of the load capacitors C<sub>L1</sub> and C<sub>L2</sub>
- the stray capacitance of the PCB paths
- the parasitic capacitance of the oscillator pins.

Any change on the capacitances listed above directly shifts the oscillation frequency. When the design is in production stage, many of these capacitance values cannot be accurately controlled. Selecting a crystal with low-pullability limits the influence of such production uncertainties on the final oscillation frequency accuracy.

Generally speaking, the higher the load capacitance of a crystal, the lower its pullability. As an example, let us consider a crystal with a pullability of 45 PPM / pF. To fine tune the oscillation frequency, this crystal is loaded by two C0G ceramic capacitors (with a  $\pm$  5% tolerance of their nominal value),  $C_{l,1}$  and  $C_{l,2}$ , with the same 7 pF capacitance.

From the crystal point of view, the two load capacitors are mounted in series, which means that their contribution to  $C_1$  is  $(C_{1,1} = C_{1,2}) / 2$ . The tolerance on their contribution to  $C_1$ 



AN2867 Rev 16 17/59

remains the same, and is equal to  $\pm$  5%. If we consider that all the remaining contributors to the  $C_L$  are maintained to their nominal values at design stage (to assess the frequency shift magnitude induced only by load capacitor tolerances), then the load capacitance seen by the crystal ( $C_L$ ) either decreases by 0.175 pF, or increases by the same value. This induces an oscillation shift of:

 $0.175 \text{ pF} \times 45 \text{ PPM} / \text{pF} = \sim 7.8 \text{ PPM} (\sim 0.7 \text{ s/day for a time-keeping function such as RTC})$ 

The above example shows that, the lower the pullability, the lower the impact of small load capacitance deviation on the frequency shifting. Crystal pullability is an important factor when defining the final application PPM budget.

$$Pullability_{(PPM/pF)} = \frac{C_m \times 10^6}{2 \times (C_0 + C_L)^2}$$

where

- C<sub>m</sub> is the crystal motional capacitance (in pF)
- C<sub>0</sub> is the crystal shunt capacitance (in pF)
- C<sub>I</sub> is the crystal nominal load capacitance (in pF)

Next sections give a more detailed description on how to calibrate the oscillation frequency and how to estimate the final accuracy uncertainty (PPM) budget.

## 3.8 Safety factor

#### 3.8.1 Definition

Resonators (such as crystal resonators) are well known to undergo aging effects that manifest themselves over time in deviations of resonator parameters from the values defined by the specifications. Among the impacted parameters there is the resonator ESR, whose value depends on the environment conditions, such as moisture and temperature. The oscillator transconductance depends upon the power supply voltage and upon the temperature.

The safety factor parameter enables to determine the oscillator safe operation under the operating conditions and during the application life. It measures the ability of the oscillator not to fail under operating conditions.

The safety factor is defined as the ratio between the oscillator negative resistance and the resonator FSR:

$$S_f = \frac{\text{Oscillator negative resistance}}{\text{Crystal ESR}} = \frac{R_{ADD} + \text{Crystal ESR}}{\text{Crystal ESR}}$$

#### 3.8.2 Measurement methodology

To measure the oscillator negative resistance, a resistance is added in series to the resonator, as indicated in *Figure 8*.

STM32

CL1

CL1

MSv37268V1

Figure 8. Negative resistance measurement methodology description

The oscillator negative resistance is the value of smallest series resistance R<sub>ADD</sub> preventing the oscillator from starting up successfully.

In practice, this value is set by conducting several experiments in which the value of the series resistance is slightly increased compared to the previous experiment. The sequence stops when the oscillator is unable to start correctly. The oscillator negative resistance is equal to the value of the added series resistance.

#### 3.8.3 Safety factor for STM32 and STM8 oscillators

*Table 4* summarizes the safety factor  $(S_f)$  for oscillators embedded in STM32 and STM8 devices. For the LSE oscillator, the oscillation is considered safe for  $S_f \ge 3$ , while for the HSE oscillator this is true when  $S_f \ge 5$ .

Table 4. Safety factor (S<sub>f</sub>) for STM32 and STM8 oscillators<sup>(1)</sup>

1. Safe and very safe oscillations are shown in green, while unsafe oscillation is show in yellow.

577

AN2867 Rev 16 19/59

#### 3.9 Oscillation modes

#### 3.9.1 What are fundamental and overtone modes?

Equation (4) gives the oscillation frequency  $F_p$  of a crystal, which depends on the series resonant frequency  $F_s$  for which the crystal impedance is null. The oscillator is said to operate in fundamental mode when vibrating around  $F_p$ .

Fs (and hence  $F_p$ ) depends upon the parameters of the crystal theoretical model illustrated in *Figure 1*. These parameters, given by the crystal manufacturer, define the frequency for which the crystal is designed to oscillate around the fundamental frequency.

In real life, an AT-cut quartz crystal impedance reaches a zero value for several frequencies, which corresponds to the odd multiples of its fundamental vibration frequency. A crystal can also vibrate around one of those odd multiples, these are the overtone oscillation modes. *Figure 9* represents the cancellation of an AT-cut crystal impedance for the fundamental frequency, its following odd multiples (third and fifth overtones are represented) as well as for some spurious frequencies.

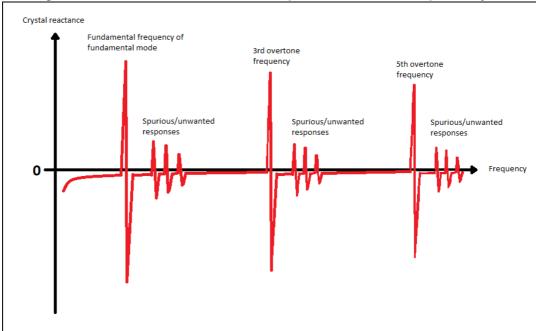


Figure 9. Fundamental and overtone frequencies of an AT-cut quartz crystal

Note:

AT-cut quartz corresponds to most of the crystals to be used with HSE. For LSE, tuning fork crystals can be used but do not show the same oscillation mode possibilities (Figure 9 is not valid for such crystals). In this part, we consider an AT-cut quartz crystal when referring to a crystal.

This multiple-time cancellation is due to the fact that a more accurate quartz crystal theoretical model shows a RLC branch for each one of its overtone modes as illustrated in *Figure 10*.

Figure 10. Quartz crystal theoretical model with third overtone

For example, it is possible to use the third overtone mode by implementing the oscillator as shown in *Figure 11*, to suppress the fundamental frequency (theoretically each overtone mode can be selected by suppressing previous ones).

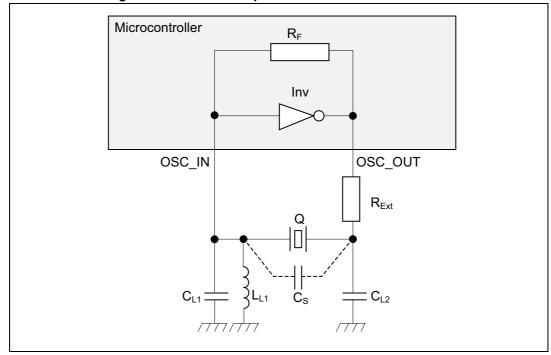


Figure 11. Oscillator implementation for third overtone

#### 3.9.2 Third overtone mode: pros and cons

Because of the thickness needed, the crystals designed for a high frequency fundamental mode are very expensive, and require high-end cutting technologies and a lot of caution for implementation. Practically, it becomes impossible to operate in fundamental mode for a frequency above 50 MHz. This is why most of the high frequency crystals are designed to work in the third overtone mode (it is possible to cut the crystal for a three times lower frequency than the one it oscillates at).

AN2867 Rev 16 21/59

The model for a crystal operating in third overtone mode (Figure~11) shows approximately a resistance  $R_m$  three times higher and a capacitance  $C_m$  nine times lower than those associated to the fundamental mode.

For the third overtone mode, these differences mean a higher Q-factor since the quality factor for an RC series circuit is  $1/\omega$ RC (less energy loss, more stable performances, better jitter, and lower pullability, see *Section 3.7*). A lower pullability means less frequency shifting when the application is deployed in the field but also a lower tunability of the oscillation frequency.

#### 3.9.3 Considerations for crystals interfaced with STM32 products

The oscillators integrated in the STM32 products have been validated for use in the fundamental mode, respecting the implementation of *Figure 5*. If a third overtone crystal is used with this implementation, the theory indicates that it does not start vibrating at the third harmonic frequency, but at the fundamental one.

Note:

The start-up mode of an oscillator can even involuntarily balance between the two modes if its external components have not been chosen according to what indicated in this document.



## 4 Guidelines to select a suitable crystal and external components

### 4.1 Low-speed oscillators embedded in STM32 MCUs / MPUs

The low-speed resonator market provides a wide range of crystal resonators. Selecting the most adequate one for a given design depends on many parameters. Below a list of the most important parameters to be taken into account (only technical factors are listed):

- · Crystal size or footprint
- Crystal load capacitance (C<sub>I</sub>)
- Oscillation frequency offset (PPM)
- Start-up time.

A trade-off between the above parameters must be found depending on the key design criteria. *Figure 12* shows that the resonators available on the market can be divided into two categories, depending on the above mentioned factors and trade-offs.

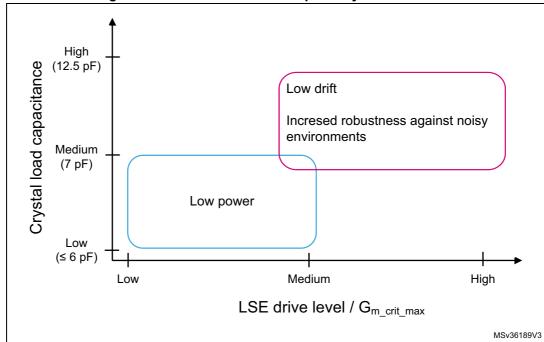


Figure 12. Classification of low-speed crystal resonators

A resonator with a relatively high load-capacitance (such as 12.5 pF) requires more power for the oscillator to drive the oscillation loop at the resonator nominal frequency. Designs targeting low power consumption (e.g. RTC application powered by coin-batteries requiring very long autonomy) are consequently more likely to use resonators with relatively small load capacitance. On the other side, big load capacitance resonators have a much smaller pullability compared to resonators with small load capacitance. As a result, designs without severe constraints on power consumption tend to use big load capacitance crystals to reduce pullability.

One of the key areas where crystal resonators are massively used is the hand-held and wearable appliance consumer market (e.g. smartphones, Bluetooth<sup>®</sup> kits). For this market

57

AN2867 Rev 16 23/59

segment the crystal size is of critical importance. However, it is widely known that smallfootprint crystals come with high crystal ESR. For this kind of designs, the choice may be harder if the target design has severe constraints in terms of power consumption (the usual scenario). In this case, choose a crystal with a load capacitance as small as possible to optimize power consumption even if this compromises pullability. In addition, crystals with high ESR may have a slightly longer start-up time. If there are no constraints on crystal size, then it is recommended to choose a crystal with the smallest possible ESR.

In noisy environment (almost always the case for industrial applications), if there are no constraints on power consumption, it is recommended to choose crystals with high load capacitance. These crystals require a high-drive current from the oscillator while being more robust against noise and external perturbations. Another advantage is that the design pullability is minimized.

Depending on the used device, all the resonator families listed below can be compatible with your design, or only some of them. STM32 devices embed two types of low-speed oscillator (LSE):

Constant-gain low-speed oscillators

This type of LSE oscillators features a constant gain, which makes them compatible only with a few crystal groups mentioned above. For example, LSE oscillators embedded in STM32F2 and STM32L1 microcontrollers target designs with severe power consumption constraint. The selected crystal should consequently have a low load capacitance and a moderate ESR. LSE oscillators embedded into STM32F1 microcontrollers target crystal resonators with moderate ESR and moderate load capacitance.

Configurable-gain low-speed oscillators

LSE oscillators belonging to this family have the main advantage to be compatible with a large number of crystals. Almost no constraint is by the STM32 device embedding this kind of LSE oscillator. This large list of compatible resonator crystals allows the designer to focus only on design constraints (such as power consumption, footprint) when selecting a compatible resonator. These LSE oscillators are divided into two categories:

- Dynamically (on-the-fly) modifiable gain LSE oscillators The gain of this type of LSE oscillators can be changed either before starting the oscillator or after enabling it.
- Statically modifiable gain LSE oscillators The gain can be changed only when the LSE oscillator is turned off. If the oscillator transconductance has to be increased or decreased, the LSE must be turned off first.

Table 5 gives the list of low-speed oscillators (LSE) embedded in STM32 devices.

Caution: When the gain is modified either statically or on-the-fly, the calibration of the oscillation frequency must be re-adjusted to estimate the final accuracy uncertainty (PPM) budget.

Caution: In STM32F0 and STM32F3 MCUs, High drive mode ( $g_m = 25 \mu A/V$ ) must be used only with 12.5 pF crystals, to avoid saturating the oscillation loop and causing a start-up failure. When used with a low C<sub>1</sub> crystal (for example 6 pF), the oscillation frequency jitters and duty cycle may be distorted.



#### Table 5. LSE oscillators embedded into STM32 MCUs/MPUs<sup>(1)</sup>

	Table of Lot occurred different file of file of																		
Series	F0, F3 F1, T F2 F4_g1 <sup>(2)</sup> F4_g2 <sup>(3)</sup> F7			F1, T F2 F4_g1 <sup>(2)</sup>			L1	L0, L4, L4+, L5, G0, G4, H7, MP1, WB, WL, U5 <sup>(4)</sup>			11								
Drive level	Low	Medium low	Medium high	High	N	ot availab	ole	Low	High	Low	Medium low	Medium high	High	Not available	Low	Medium low	Medium high	High	Unit
9 <sub>m (min)</sub>	5	8	15	25	5	2.8	2.8	2.8	7.5	2.4	3.75	8.5	13.5	3	2.5	3.75	8.5	13.5	μA / V
G <sub>m_crit_max</sub>	1	1.6	3	5	1	0.56	0.56	0.56	1.5	0.48	0.75	1.7	2.7	0.6	0.5	0.75	1.7	2.7	μ

- 1. Color code:
  - Light blue: LSE oscillators with transconductance modifiable on the fly (dynamically)
     Yellow: LSE oscillators with non-modifiable transconductance
     Gray: LSE oscillators with statically-modifiable transconductance
- 2. F4\_g1: STM32F4 Series with LSE generation 1. This category corresponds to STM32F401/405/ 407/415/417/427/429/437/439xx MCUs featuring LSE oscillators with non-modifiable transconductance.
- 3. F4\_g2: STM32F4 Series with LSE generation 2. This category corresponds to STM32F410/411/412/413/423/446/469/479xx MCUs featuring LSE oscillators with statically-modifiable transconductance.
- 4. STM32U5 Series does not support Low drive mode.

AN2867 Rev 16

## 4.2 How to select an STM32-compatible crystal

This section describes the procedure recommended to select suitable crystal/external components. The procedure is based on the following steps:

#### Step 0: Choose a fundamental mode designed resonator

Choose a fundamental mode designed resonator (as explained in Section 3.9, the STM32 oscillators are validated to work with resonator vibrating in fundamental mode and while using the Pierce oscillator circuitry presented in Figure 5), and make sure that the resonator chosen is designed to work in fundamental mode.

#### Step 1: Check the resonator compatibility with the selected STM32

To check the compatibility between the selected crystal and the STM32 MCU / MPU, first identify which procedure has to be followed among the two described in *Section 3.4*. The decision must be made based on the oscillator specification provided in the datasheet.

- If the oscillator transconductance parameter is specified, then apply the second procedure. Ensure that the gain margin ratio is higher than five (x5) to make sure that the crystal is compatible with the selected STM32 part.
- If  $G_{m\_crit\_max}$  is specified instead, make sure that gmcrit for the oscillation loop is smaller than the specified  $G_{m\_crit\_max}$  value.

#### Step 2: Determine the capacitance value of the load capacitors $C_{L1}$ and $C_{L2}$

To determine the correct capacitance values for  $C_{L1}$  and  $C_{L2}$  load capacitors, apply the formula specified in *Section 3.3*. The values obtained are approximations of the exact capacitances to be used. In a second phase, to fine tune the values of the load capacitors, go through a series of experimental iterations, until the right capacitance values are found.

During the experimental phase, use a standard crystal, one whose PPM drift is well known when it is loaded by the crystal nominal load capacitance ( $C_L$ ). This kind of crystals can be provided by the manufacturer upon request. After this crystal has been chosen, calculate its oscillation frequency ( $F_{standard}$ ) when the crystal is loaded by its nominal load capacitance. This frequency is given by the formula:

$$F_{standard} = F_{nominal} \times (PPM_{standard} / 10^6)$$

#### where:

- F<sub>standard</sub> is the standard crystal oscillation frequency when it is loaded by its nominal load capacitance
- F<sub>nominal</sub> is the oscillation nominal frequency specified in the crystal datasheet
- PPM<sub>standard</sub> is the oscillation frequency drift of the standard crystal, as characterized by the crystal manufacturer

When F<sub>standard</sub> is computed, go through the following sequence:

- Make the first experimental iteration with C<sub>L1</sub> and C<sub>L2</sub> capacitance values determined by calculation:
  - If the oscillation frequency is equal to F<sub>standard</sub>, C<sub>L1</sub> and C<sub>L2</sub> are the correct capacitances. User can therefore skip sub-steps 2 and 3.
  - If the oscillation frequency is slower than F<sub>standard</sub> go to sub-step 2, otherwise execute sub-step 3.
- 2. For this experimental iteration, decrease  $C_{L1}$  and  $C_{L2}$  capacitance values, measure again the oscillation frequency, and compare it to  $F_{standard}$ :
  - If the oscillation frequency is slower than F<sub>standard</sub>, execute sub-step 2, otherwise execute sub-step 3.
  - If the oscillation frequency is almost equal to F<sub>standard</sub>, use the latter C<sub>L1</sub> and C<sub>L2</sub> capacitance values.
- For this experimental iteration, increase C<sub>L1</sub> and C<sub>L2</sub> capacitance values, measure again the oscillation frequency, and compare it to F<sub>standard</sub>:
  - If the oscillation frequency is slower than F<sub>standard</sub>, execute sub-step 2, otherwise execute sub-step 3.
  - If the oscillation frequency is almost equal to  $F_{standard}$ , use the latter  $C_{L1}$  and  $C_{L2}$  capacitance values.

#### Step 3: Check the safety factor of the oscillation loop

The safety factor must be assessed as described in *Section 3.8* to ensure a safe oscillation of the oscillator under operating conditions.

Note:

Many crystal manufacturers can check microcontroller / crystal pairing compatibility upon request. If the pairing is judged valid, they can provide a report including the recommended  $C_{L1}$  and  $C_{L2}$  values, as well as the oscillator negative resistance measurement. In this case steps 2 and 3 can be skipped.

#### Step 4: Calculate the drive level and external resistor

Compute the drive level (DL) (see *Section 3.5*) and check if it is greater or lower than DL<sub>crystal</sub>:

- If DL < DL<sub>crystal</sub>, no need for an external resistor (a suitable crystal has been found).
- If DL > DL<sub>crystal</sub>, user should calculate R<sub>Ext</sub> to have: DL < DL<sub>crystal</sub>. User should then recalculate the gain margin taking R<sub>Ext</sub> into account.
   If gain margin > 5, a suitable crystal has been found. If not, then this crystal does not work, another one must be chosen. Return to Step 1: Check the resonator compatibility with the selected STM32 to run the procedure for the new crystal.

#### Step 5 (optional): Calculate the PPM accuracy budget

Finally, use the formula below to estimate the PPM accuracy budget for the application:

$$PPM_{Budget} = PPM_{crystal} + Deviation(C_L) \times Pullability_{crystal}$$

where:

- PPM<sub>Budget</sub> is the estimated accuracy for the oscillation frequency
- PPM<sub>crvstal</sub> is the crystal PPM accuracy specified in the datasheet



AN2867 Rev 16 27/59

Deviation ( $C_L$ ) is expressed in pF. It measures the deviation of the load capacitance ( $C_L$ ) due to tolerances on load capacitor values and the variation of the stray capacitance ( $C_S$ ) due to PCB manufacturing process deviation.

Pullabilty is expressed in PPM / pF (refer to Section 3.7).

Note:

The PPM budget calculated above does not take into account the temperature variation, which can make the PPM budget bigger.



#### Recommended resonators for STM32 MCUs/MPUs 5

#### 5.1 STM32-compatible high-speed resonators

The high-speed oscillator (HSE) embedded into STM32 products<sup>(a)</sup> is compatible with almost all the resonators available on the market. They are provided by a wide range of manufacturers, including:

- **ABRACON**
- EPSON (http://www5.epsondevice.com)
- **KYOCERA**
- Micro Crystal
- muRata (www.murata.com)
- NDK (http://www.ndk.com)
- RIVER (http://www.river-ele.co.jp)

Compatible resonators have various frequencies and technologies (ceramic resonators and quartz-crystal resonators working in fundamental mode are all compatible with the HSE oscillator embedded in STM32 MCUs/MPUs). Table 6 summarizes the supported frequency ranges.

Table 6. HSE oscillators embedded in STM32 MCUs/MPUs

Series	STM32F0 STM32F3	STM32F1 STM32T	STM32F2	STM32F4	STM32F7	STM32L0	STM32L1	STM32L4 STM32L4+ STM32L5 STM32H7 STM32G0 STM32G4 STM32MP1	STM32U5	Unit
Frequency range	4 - 32	4 - 16	4 - 25	4 - 26	4 - 26	1 - 25	1 - 24	4 - 48	4 - 50	MHz
9 <sub>m (min)</sub>	10	25	5	5	5	3.5	3.5	7.5	7.5	mA/V
G <sub>m_crit_max</sub>	2	5	1	1	1	0.7	0.7	1.5	1.5	IIIAV V

#### 5.2 STM32-compatible low-speed resonators

Table 7 contains a not exhaustive set (only the compatible resonator part-numbers checked by STMicroelectronics are listed) of low-speed quartz-crystal 32.768 kHz resonators that are either compatible with the whole STM32 portfolio or with a subset. Different footprints are provided to facilitate crystal selection even if there are geometric constraints for the final application.

a. This is not applicable for STM32WB and STM32WL Series due to the RF constraints. For information about HSE oscillator compatibility with STM32WB and STM32WLSeries, refer to Precise HSE frequency and startup time tuning for STM32 wireless MCUs (AN5042) available on www.st.com.



AN2867 Rev 16 29/59

AN2867

Table 7. Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products

Package size (mm²)	Manufacturer	Quartz ref / Part number	ESR max (kΩ)	C <sub>0</sub> (pF)	C <sub>L</sub> (pF)	g <sub>mcrit</sub> <sup>(1)</sup> (μΑ/V)	STM32 Series compatibility <sup>(2)(3)</sup>
0.95 x 0.6		WMRAG32K76CS1C00R0					F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		WMRAG32K76CS2C00R0			8	0.8144	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	muRata	WMRAG32K76CS3C00R0	75	0.003	0	0.0144	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	IlluRala	WMRAG32K76CS4C00R0	75	0.003			F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		WMRAG32K76CT2C00R0			9	1.0308	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		WMRAG32K76CV2C00R0			12.5	1.9880	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
RIVER				5	0.6447	F0, F1, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1	
	DIV/ED	TEV 05V	90	1.5	7	1.1026	F0, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
	RIVER	TFX-05X	90		9	1.6824	F0, F3, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
					12.5	2.9910	F0, F3
	SII	SC-12S (2 terminals)		1.4	6	0.8356	F0, F1, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1
			90		7	1.0768	F0, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
					9	1.6506	F0, F3, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
					12.5	2.9484	F0, F3
		ECS327-7-1210-TR		1.1	7	1.0012	F0, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
1.2 x 1.0		ECS327-9-1210-TR	90		9	1.5567	F0, F3, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-12.5-1210-TR			12.5	2.8225	F0, F3
	ECS	ECS327-5-1210B-CN-TR		1.5	5	0.5731	F0, F1, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1
		ECS327-7-1210B-CN-TR	00		7	0.9800	F0, F1, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-9-1210B-CN-TR	- 80		9	1.4955	F0, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-12.5-1210B-CN-TR			12.5	2.6587	F0, F3, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ABS04W-32.768 KHz 4 pF			4	0.4103	F0, F1, F2, F3, F4, L0, L1, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1
	ADDACON	ABS04W-32.768 KHz 6 pF	80	1.5	6	0.7630	F0, F1, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1
	ABRACON	ABS04W-32.768 KHz 9 pF	00	1.5	9	1.4955	F0, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ABS04W-32.768 KHz 12.5 pF			12.5	2.6587	F0, F3, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5

۷I	ı
	ı
	'

Table 7. Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products (continued)

Package size (mm²)	Manufacturer	Quartz ref / Part number	ESR max (kΩ)	C <sub>0</sub> (pF)	C <sub>L</sub> (pF)	g <sub>mcrit</sub> <sup>(1)</sup> (μΑ/V)	STM32 Series compatibility <sup>(2)(3)</sup>
		CM9V-T1A / CM9V-T1A 0.3	90	1.4	4	0.4449	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
					6	0.8356	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	Micro Crystal				7	1.0768	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
					9	1.6506	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
					12.5	2.9484	F0, F3
		ECS327-6.5-16-TR		1.3	6.5	0.9284	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	ECS	ECS327-9-16-TR			9	1.6190	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-12.5-16-TR			12.5	2.9062	F0, F3
	NDK -	NX1610SA 32.768 kHz EXS00A-MU00658		1.3	6	0.8132	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		NX1610SA 32.768 kHz EXS00A-MU01367			12.5	2.9062	F0, F3
		NX1610SE 32.768 kHz EXS00A-MU01501	60 <sup>(4)</sup>	1.55	6	0.5799	F0, F1, F2, F3, F4, L0, L1, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1
1.6 x 1.0		NX1610SE 32.768 kHz EXS00A-MU01500			7	0.7437	F0, F1, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
		NX1610SE 32.768 kHz EXS00A-MU01499			9	1.1323	F0, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
		NX1610SE 32.768 kHz EXS00A-MU01498			12.5	2.0083	F0, F3, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
	SII	SC-16S		4.0	6	0.7910	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
				1.2	12.5	2.8642	F0, F3
	FDOON	FC1610AN 32.768000 kHz 9		1.2	9	1.5877	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	EPSON -	FC1610AN 32.768000 kHz 12.5	90		12.5	2.8642	F0, F3
	CITIZEN	CM1610H		1.2	6	0.7910	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
					7	1.0261	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
					9	1.5877	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
					12.5	2.8642	F0, F3

AN2867 Rev 16

Recommended resonators for STM32 MCUs/MPUs

Table 7. Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products (continued)

Package size (mm²)	Manufacturer	Quartz ref / Part number	ESR max (kΩ)	C <sub>0</sub> (pF)	C <sub>L</sub> (pF)	g <sub>mcrit</sub> <sup>(1)</sup> (μΑ/V)	STM32 Series compatibility <sup>(2)(3)</sup>
	ABRACON	ABS05-32.768 kHz 9 pF	- 90	1.3	9	1.6190	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ABS05-32.768 kHz			12.5	2.9062	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ABS05W-32.768 kHz-D	70	2	4	0.4272	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
				1.3	5	0.6056	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		TFX-04	90		7	1.0513	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
1.6 x 1.0		11 X-0 <del>4</del>	90		9	1.6190	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	RIVER -				12.5	2.9062	F0, F3
	RIVER	TFX-04C	60	1.5	5	0.4298	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
					7	0.7350	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
					9	1.1216	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
					12.5	1.9940	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	ABRACON -	ABS06L-32.768kHz-9pF	100	-	9	1.3734	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ABS06L-32.768kHz			12.5	2.6494	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ABS06W-32.768kHz-D	95	1	3	0.2577	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ABS06-127-32.768kHz		_	12.5	2.3844	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ABS06-32.768kHz-4P			4	0.2441	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ABS06-32.768kHz-6	90		6	0.5493	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
2.0 x 1.2		ABS06-32.768kHz-7	90		7	0.7477	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
2.0 X 1.2		ABS06-32.768kHz-9			9	1.2361	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ABS06-32.768kHz			12.5	2.3844	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ABS06-107-32.768kHz-T	80	1.5	4	0.4103	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	ECS -	ECS327-6-12L-TR		1.3	6	0.9035	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ECS327-7-12L-TR	100		7	1.1681	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-9-12L-TR			9	1.7988	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	[	ECS327-12.5-12L-TR			12.5	3.2299	F0, F3

Table 7. Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products (continued)

Package size (mm²)	Manufacturer	Quartz ref / Part number	ESR max (kΩ)	C <sub>0</sub> (pF)	C <sub>L</sub> (pF)	g <sub>mcrit</sub> <sup>(1)</sup> (μΑ/V)	STM32 Series compatibility <sup>(2)(3)</sup>
	-	ECS327-6-12L-TR	100	1.3	6	0.9035	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ECS327-7-12L-TR			7	1.1681	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-9-12L-TR			9	1.7988	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-12.5-12L-TR			12.5	3.2299	F0, F3
	ECS -	ECS327-6-12-TR	90		6	0.8312	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ECS327-7-12-TR			7	1.0513	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-9-12-TR			9	1.6190	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
2.0 x 1.2		ECS327-12.5-12-TR			12.5	2.9062	F0, F3
2.0 X 1.2		ECS327-CDX-1082	80	1.5	4	0.4103	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ECS327-6-12RR-TR		1.7	6	0.7372	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ECS327-7-12RR-TR			7	0.8983	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-9-12RR-TR		1.7	9	1.3589	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-12.5-12R-TR	70		12.5	2.3933	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-6-12R-TR	]		6	0.4517	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ECS327-9-12R-TR		1.3	9	0.8994	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-12.5-12R-TR			12.5	1.6145	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5

AN2867 Rev 16

4/59	Package size (mm²)	Manufacturer	Quartz ref / Part number	ESR max (kΩ)	C <sub>0</sub> (pF)	C <sub>L</sub> (pF)	g <sub>mcrit</sub> <sup>(1)</sup> (μΑ/V)	STM32 Series compatibility <sup>(2)(3)</sup>
			CM8V-T1A 0.3	90		4	0.4126	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
						6	0.7910	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
						7	1.0261	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
						9	1.5877	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
						12.5	2.8642	F0, F3
				80	1.2	4	0.3667	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
						6	0.7031	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		Micro Crystal	CC8V-T1A			7	0.9120	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	2.0 x 1.2					9	1.4113	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
_						12.5	2.5460	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
AN2867 Rev 16			CM8V-T1A	70		4	0.3209	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
367						6	0.6152	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
Rev						7	0.7980	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
16						9	1.2349	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
						12.5	2.2277	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		EPSON	FC-12M 32.768000kHz 12.5	90	1.3	12.5	2.9062	F0, F3
			FC-12D 32.768000kHz 7	75	0.8	7	0.7737	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
			FC-12D 32.768000kHz 9			9	1.2213	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
			FC-12D 32.768000kHz 12.5			12.5	2.2495	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		RIVER		90	1.3	5	0.6447	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
			TFX-03			7	1.0513	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
						9	1.6190	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
						12.5	2.9062	F0, F3
			TFX-03C	60	1.8	5	0.4704	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
						7	0.7878	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
7						9	1.1866	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
1 7						12.5	2.0804	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5

Table 7. Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products (continued)

AN2867 Rev 16

Table 7. Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products (continued)

Package size (mm <sup>2</sup> )	Manufacturer	Quartz ref / Part number	ESR max (kΩ)	C <sub>0</sub> (pF)	C <sub>L</sub> (pF)	g <sub>mcrit</sub> <sup>(1)</sup> (μΑ/V)	STM32 Series compatibility <sup>(2)(3)</sup>
	KYOCERA -	ST2012SB 32768 Z0	80	1.3	4	0.3810	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ST2012SB 32768 A0			5	0.5383	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ST2012SB 32768 B0			6	0.7228	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ST2012SB 32768 C0			7	0.9344	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ST2012SB 32768 E0			9	1.4391	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ST2012SB 32768 H5			12.5	2.5833	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	NDK	NX2012SA 32.768 kHz EXS00A-MU00527		1.3	6	0.7228	F0, F1, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1
		NX2012SA 32.768 kHz EXS00A-MU00524	80		7	0.9344	F0, F1, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
		NX2012SA 32.768 kHz EXS00A-MU00528			12.5	2.5833	F0, F3, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
2.0 x 1.2		NX2012SE 32.768 kHz EXS00A-MU01260	- 50 <sup>(4)</sup>	1.7	6	0.5026	F0, F1, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1
		NX2012SE 32.768 kHz EXS00A-MU01259			7	0.6416	F0, F1, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
		NX2012SE 32.768 kHz EXS00A-MU01611			9	0.9706	F0, F1, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
		NX2012SE 32.768 kHz EXS00A-MU01612			12.5	1.7095	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		SC-20T	75	1	6	0.6231	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	SII -				7	0.8138	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
					9	1.2717	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
					12.5	2.3177	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		SC-20S	70	1.3	6	0.6325	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		00-200	70	1.0	12.5	2.2604	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5

36/59 Table 7. Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products (continued) g<sub>mcrit</sub><sup>(1)</sup> Package **ESR** max  $C_0$ STM32 Series compatibility<sup>(2)(3)</sup> Manufacturer Quartz ref / Part number size (mm<sup>2</sup>)  $(k\Omega)$ (pF) (pF) (µA/V) 0.6325 F0, F1, F3, F4\_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1 7 0.8176 F0, F1, F3, F4 g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5 2.0 x 1.2 CITIZEN CM2012H 70 1.3 9 1.2592 F0, F3, F4\_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5 12.5 2.2604 F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5 ST3215SB 32768 Z0 4 0.2849 F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1 ST3215SB 32768 A0 0.4131 F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1 ST3215SB 32768 B0 0.5650 F0, F1, F3, F4\_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1 **KYOCERA** 70 0.9 ST3215SB 32768 C0 0.7407 F0, F1, F3, F4\_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5 ST3215SB 32768 E0 1.1633 F0, F3, F4\_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5 AN2867 Rev 16 ST3215SB 32768 H5 12.5 2.1312 F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5 7 ABS07L-32.768kHz 7pF 0.9751 F0, F1, F3, F4\_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5 ABS07L-32.768kHz 9pF 80 1.4 1.6472 F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5 3.2 x 1.5 ABS07L-32.768kHz 12.5 2.6208 F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5 ABS07-32.768kHz 6pF 0.5815 F0, F1, F3, F4, g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1 ABS07-32.768kHz 7pF 7 0.7596 F0, F1, F3, F4, q2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5 **ABRACON** ABS07-32.768kHz 9pF 70 11 9 1.1869 F0, F3, F4 g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5 ABS07 32.768kHz 12.5 2.1631 F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5 ABS07-166-32.768kHz-T 7 0.7596 F0, F1, F3, F4\_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5 1.2 6 0.5273 ABS07-120-32.768kHz-T 60 F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1

ABS07W-32.768kHz-D

ABS07-LR-32.768 kHz-6

55

50

1.15

1.3

3

0.1606

0.4517

F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1

F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1

1
-

Table 7. Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products (continued)

1	Package size (mm²)	Manufacturer	Quartz ref / Part number	ESR max (kΩ)	C <sub>0</sub> (pF)	C <sub>L</sub> (pF)	g <sub>mcrit</sub> <sup>(1)</sup> (μΑ/V)	STM32 Series compatibility <sup>(2)(3)</sup>
						6	0.5733	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
			CM315D		0,95	7	0.7501	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
			ONIOTOD		0,55	9	1.1751	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
						12.5	2.1471	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
				70		4	0.2678	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
						6	0.5407	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		CITIZEN	CM315E		0,75	8	0.9087	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
						9	1.1283	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
						12.5	2.0838	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
_			CM315DL	50	1,3	6	0.4517	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
AN2867 Rev 16						7	0.5840	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
867						9	0.8994	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
Rev	3.2 x 1.5					12.5	1.6145	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
6			CC7V-T1A CM7V-T1A (low profile)	70	1,2	6	0.6152	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
						7	0.7980	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
						9	1.2349	F0, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
						12.5	2.2277	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
						6	0.5571	F0, F1, F2, F3, F4, L0, L1, L4, L5, G0, G4, F7, H7, WB, WL, MP1
		Micro Crystal	CM7V-T1A 0.3	60		7	0.7178	F0, F1, F3, F4_g2, L0, L4, L5, G0, G4, F7, H7, WB, WL, MP1, U5
		WIICIO CIYSIAI	CIVI7 V-1 1A 0.3	60	1,4	9	1.1004	F0, F3, F4_g2, L0, L4, L5, G0, G4, F7, H7, WB, WL, MP1, U5
						12.5	1.9656	F0, F3, L0, L4, L5, G0, G4, F7, H7, WB, WL, MP1, U5, U5
						6	0.4517	F0, F1, F2, F3, F4, L0, L1,L4, L5, G0, G4, F7, H7, WB, WL, MP1
			CM7V-T1A	50	1 2	7	0.5840	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
			CIVIT V-1 1A	50	1,3	9	0.8994	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
37						12.5	1.6145	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5

Table 7. Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products (continued)

Package size (mm²)	Manufacturer Quartz ref / Part number		ESR max (kΩ)	C <sub>0</sub> (pF)	C <sub>L</sub> (pF)	g <sub>mcrit</sub> <sup>(1)</sup> (μΑ/V)	STM32 Series compatibility <sup>(2)(3)</sup>
		FC-135 32.768000 kHz 7			7	0.7596	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		FC-135 32.768000 kHz 9		1	9	1.1869	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		FC-135 32.768000 kHz 12.5	70		12.5	2.1631	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	EPSON	FC-13A 32.768000 kHz 9		0.9	9	1.1633	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		FC-13A 32.768000 kHz 12.5			12.5	2.1312	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
3.2 x 1.5		FC-135R 32.768000 kHz 7	50	1.1	7	0.5562	F0, F1, F3, F4_g2, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
3.2 X 1.5		FC-135R 32.768000 kHz 9			9	0.8648	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		FC-135R 32.768000 kHz 12.5			12.5	1.5681	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		SC-32S	70		6	0,5815	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	SII	30-323	70	1	12.5	2.1631	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	SII	SC-32P 5	50	'	6	0,4154	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
			50		12.5	1.5451	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5

Table 7. Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products (continued)

Package size (mm²)	Manufacturer	Quartz ref / Part number	ESR max (kΩ)	C <sub>0</sub> (pF)	C <sub>L</sub> (pF)	g <sub>mcrit</sub> <sup>(1)</sup> (μΑ/V)	STM32 Series compatibility <sup>(2)(3)</sup>
		ECS327-6-34QS-TR			6	0.5983	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ECS327-7-34QS-TR		1 1	7	0.7787	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-9-34QS-TR		1,1	9	1.2108	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-12.5-34QS-TR			12.5	2.1953	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-6-34G-TR		0,75	6	0.5407	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ECS327-12.5-34G-TR	70	0,75	12.5	2.0838	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-6-34S-TR	70		6	0.5899	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	ECS -	ECS327-12.5-34S-TR		1,05	12.5	2.1792	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECX327-CDX-1293			12.5	2.1792	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
3.2 x 1.5		ECS327-7-34B-TR			7	0.7691	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
3.2 X 1.5		ECS327-9-34B-TR			9	1.1988	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-12.5-34B-TR			12.5	2.1792	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-CDX-1128	60	2	6	0.6511	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ECS327-6-34R-TR			6	0.4517	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ECS327-7-34R-TR	50		7	0.5840	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-9-34R-TR	30		9	0.8994	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-12.5-34R-TR		1,3	12.5	1.6145	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-6-34RR-TR			6	0.3614	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ECS327-9-34RR-TR	40		9	0.7195	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-12.5-34RR-TR			12.5	1.2916	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5

AN2867 Rev 16

Table 7. Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products (continued)

Package size (mm²)	Manufacturer	Quartz ref / Part number	ESR max (kΩ)	C <sub>0</sub> (pF)	C <sub>L</sub> (pF)	g <sub>mcrit</sub> <sup>(1)</sup> (μΑ/V)	STM32 Series compatibility <sup>(2)(3)</sup>
		NX3215SA 32.768 kHz EXS00A-MU00525			6	0.5815	F0, F1, F2, F3, F4, L0, L1, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1
		NX3215SA 32.768 kHz EXS00A-MU00523	70	1.0	7	0.7596	F0, F1, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
3.2 x 1.5	NDK	NX3215SA 32.768 kHz EXS00A-MU00526			12.5	2.1631	F0, F3, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
		NX3215SE 32.768 KHz EXS00A-MU00990	40	1.3	6	0.3323	F0, F1, F2, F3, F4, L0, L1, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1
		NX3215SE 32.768 KHz EXS00A-MU00989	40	1.5	12.5	1.2361	F0, F3, F4_g2, L0, L4, L4+, L5, G0, G4, F7, H7, WB, WL, MP1, U5
					6	0.6152	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	Micro Crystal	CC5V-T1A		1.2	7	0.7980	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
					9	1.2349	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
4.1 x 1.5					12.5	2.2277	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
4.1 X 1.5	ECS -	ECS327-6-49-TR	1.	1.1	6	0.5983	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		ECS327-7-49-TR			7	0.7787	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	LOS	ECS327-9-49-TR			9	1.2108	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-12.5-49-TR	70		12.5	2.1953	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
			70		6	0.6412	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	CITIZEN	CM519		1.35	7	0.8274	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	CITIZEN	CIVIST9		1.33	9	1.2714	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
4.9 x 1.8					12.5	2.2768	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
4.9 X 1.0		ECS327-6-39-TR			6	0.6377	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	ECS -	ECS327-7-39-TR		1.33	7	0.8235	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-9-39-TR		1.55	9	1.2665	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-12.5-39-TR			12.5	2.2702	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
6.9 x 1.4	ABRACON	ABS13 -32.768kHz-7pF	65		7	0.5400	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
6.9 X 1.4	ABRACON	ABS13 -32.768kHz	0.5	-	12.5	1.7221	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5



AN2867 Rev 16

Table 7. Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products (continued)

Package size (mm²)	Manufacturer Quartz ref / Part number		ESR max (kΩ)	C <sub>0</sub> (pF)	C <sub>L</sub> (pF)	g <sub>mcrit</sub> <sup>(1)</sup> (μΑ/V)	STM32 Series compatibility <sup>(2)(3)</sup>
		SSP-T7-F			7	0.6878	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		33P-1 <i>1-</i> F			12.5	1.9790	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	SII			0.9	3.7	0.2332	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
		SSP-T7-FL			4.4	0.3095	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
					6	0.5247	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	EPSON	MC-164 32.768000kHz 7		0.8	7	0.6705	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		MC-164 32.768000kHz 9			9	1.0585	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
7.0 x 1.5		MC-164 32.768000kHz 12.5	65		12.5	1.9496	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
7.0 X 1.5		ECS327-6-38-TR	05		6	0.5096	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	ECS	ECS327-7-38-TR			7	0.6705	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	LCS	ECS327-9-38-TR			9	1.0585	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		ECS327-12.5-38-TR			12.5	1.9496	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
				- -	6	0.5096	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	CITIZEN	CM130			7	0.6705	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
					9	1.0585	F0, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
					12.5	1.9496	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5

AN2867 Rev 16

Package size (mm²)	Manufacturer Quartz ref / Part number		ESR max (kΩ)	C <sub>0</sub> (pF)	C <sub>L</sub> (pF)	g <sub>mcrit</sub> <sup>(1)</sup> (µA/V)	STM32 Series compatibility <sup>(2)(3)</sup>
	ECS	ECS327-6-17X-TR			6	0.4580	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	ECS	ECS327-12.5-17X-TR			12.5	1.6263	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
				1.35	6	0.4580	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	CITIZEN	CM200C		1.35	7	0.5911	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	CITIZEN	CM200C	50		9	0.9081	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
8.0 x 3.8					12.5	1.6263	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	EPSON	MC-306 32.768000kHz 7		0.9	7	0.5291	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		MC-306 32.768000kHz 9			9	0.8309	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		MC-306 32.768000kHz 12.5			12.5	1.5223	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
	ABRACON	ABS25-32.768kHz-6-T	50	1.35	6	0.4580	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1
	ABRACON	ABS25-32.768kHz-T	- 50	1.33	12.5	1.6263	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		MC-405 32.768000kHz 7		50 0,85	7	0.5224	F0, F1, F2, F3, F4, L0, L1, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
10.4 x 4.0	EPSON	MC-405 32.768000kHz 9	50		9	0.8225	F0, F1, F3, F4_g2, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5
		MC-405 32.768000kHz 12.5			12.5	1.5110	F0, F3, L0, L4, L4+,L5, G0, G4, F7, H7, WB, WL, MP1, U5

- 1. As defined in Section 3.4: Oscillator transconductance.
- 2. F4\_g1: STM32F4 Series with LSE generation 1, corresponds to STM32F401/405/ 407/415/417/429/437/439xx MCUs featuring LSE oscillators with non-modifiable transconductance.
- 3. F4\_g2: STM32F4 Series with LSE generation 2, corresponds to STM32F410/411/412/413/423/446/469/479xx MCUs, featuring LSE oscillators with statically-modifiable transconductance.
- 4. Low\_ESR: -40 to +85 °C.

Note: MCUs of the STM32U5 Series do not support crystal / MEMS resonators with CL ≤ 6 pF.

# Recommended crystals for STM8AF/AL/S microcontrollers

# 6.1 Part numbers of recommended crystal oscillators

Table 8. KYOCERA compatible crystals (not exhaustive list)

Part number	Frequency	ESR max	C <sub>L</sub>	Drive level (DL)
CX3225GA8000D0PTVCC	8 MHz	500 Ω		
CX3225SA8000D0PTVCC	O IVII IZ	300 12		200 μW max
CX2016SA16000D0GSSCC		200 Ω		
CX2016GR16000D0GTVCC		300 Ω	8 pF	300 μW max
CX3225CA16000D0PSVCC CX3225GA16000D0PTVCC	16 MHz	100 Ω		200 μW max
CX3225SB16000D0GSSCC		80 Ω		100 μW max
CX3225SA16000D0PTVCC		60 Ω		200 μW max

Note: Contact provider regarding recommended crystals for new designs.

Table 9. NDK compatible crystals (not exhaustive list)

Part number	Frequency	ESR max	$C_L$	Drive level (DL)
NX3225GD 8MHz EXS00A-CG04874	8 MHz	500 Ω		
NX3225GA 16MHz EXS00A-CG04815	16 MHz	80 Ω	8 pF	
NX2016SA 16MHz EXS00A-CS07826	10 10112	200 Ω		
NX3225GA 24MHz EXS00A-CG04818	24 MHz	50 Ω	8 pF	200 μW max
NX2016SA 24MHz EXS00A-CS10820	24 WII 12	80 Ω	6 pF	200 μw max
NX3225GA 25MHz EXS00A-CG06750	- 25 MHz	50 Ω	8 pF	
NX2016SA 25MHz EXS00A-CS11321	23 1011 12	80 Ω	6 pF	
NX2016SA32MHz EXS00A-CS10925	32 MHz	80 Ω	6 pF	
NX1612SA 40MHz EXS00A-CS13836	40 MHz	80 Ω	6 pF	100 μW max
NX1612SA 48MHz EXS00A-CS13734	48 MHz	00 12	7 pF	100 μνν πιαχ



## 6.2 Recommended ceramic resonators

*Table 10* and *Table 11* give the references of recommended CERALOCK<sup>®</sup> ceramic resonators for the STM8A microcontrollers provided and certified by muRata.

Table 10. Recommended conditions (for consumer)

Part number	Frequency	C <sub>L</sub>
CSTCR4M00G55-R0	4 MHz	$C_{L1} = C_{L2} = 39 \text{ pF}$
CSTNE8M00G550000R0	8 MHz	$C_{L1} = C_{L2} = 33 \text{ pF}$
CSTNE16M0V530000R0	16 MHz	C <sub>L1</sub> = C <sub>L2</sub> = 15 pF

Table 11. Recommended conditions (for CAN-BUS)

Part number	Frequency	C <sub>L</sub>
CSTCR4M00G55B-R0	4 MHz	$C_{L1} = C_{L2} = 39 \text{ pF}$
CSTNE8M00G55A000R0	8 MHz	$C_{L1} = C_{L2} = 33 \text{ pF}$
CSTNE16M0V53C000R0	16 MHz	$C_{L1} = C_{L2} = 15 \text{ pF}$

# 7 Tips for improving oscillator stability

#### 7.1 PCB design guidelines

The 32 kHz crystal oscillator is an ultra-low-power oscillator (transconductance of a few  $\mu$ A/V). The low oscillator transconductance affects the output dynamics since smaller transconductance values generates a smaller oscillating current. This results in a lower peak-to-peak voltage on the oscillator outputs (from a few dozen to a few hundred mV).

Keeping the signal-to-noise ratio (SNR) below acceptable limits for a perfect operation of the oscillator means more severe constraints on the oscillator PCB design in order to reduce its sensitivity to noise.

Therefore, great care must be taken when designing the PCB to reduce as much as possible the SNR. A non-exhaustive list of precautions that should be taken when designing the oscillator PCB is provided below:

- Avoid high values of stray capacitance and inductances, as they can lead to uncontrollable oscillation (the oscillator can resonate at overtones or harmonics frequencies). Reducing the stray capacitance also decreases start-up time and improves oscillation frequency stability.
- To reduce high frequency noise propagation across the board, the MCU/MPU must have a stable power supply source, to ensure noiseless crystal oscillations. This means that well-sized decoupling capacitor must be used for powering the device.
- Mount the crystal as close as possible to the MCU/MPU, to keep tracks short, and to reduce inductive and capacitive effects. A guard ring around these connections, connected to the ground, is essential to avoid capturing unwanted noise, which can affect oscillation stability.
  - Long tracks/paths behave as antennas for a given frequency spectrum, generating oscillation issues when passing EMI certification tests. Refer to *Figure 14* and *Figure 16*.
- Any path conveying high-frequency signals must be routed away from the oscillator paths and components. Refer to Figure 14.
- The oscillator PCB must be underlined with a dedicated underneath ground plane, distinct from the application PCB ground plane. The oscillator ground plane should be connected to the nearest MCU/MPU ground. It prevents interferences between the oscillator components and other application components (e.g. crosstalk between paths). If a crystal in a metallic package is used, do not connect it to the oscillator ground. Refer to Figure 13, Figure 14 and Figure 15.
- Leakage current can increase start-up time and even prevent the oscillator start. If the
  device operates in a severe environment (high moisture/humidity ratio) an external
  coating is recommended.



AN2867 Rev 16 45/59

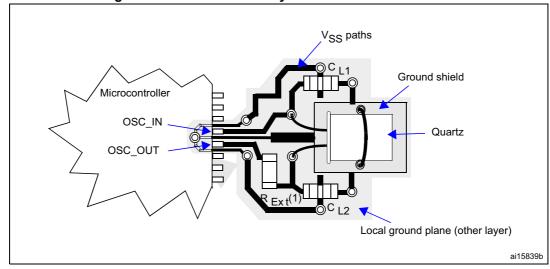


Figure 13. Recommended layout for an oscillator circuit


Warning:


It is highly recommended to apply conformal coatings to the PCB area shown in *Figure 13*, especially for the LSE quartz, CL1, CL2, and paths to the OSC\_IN and OSC\_OUT pads as a protection against moisture, dust, humidity, and temperature extremes that may lead to start-up problems.


# 7.2 PCB design examples

#### Example 1

Figure 14. PCB with separated GND plane and guard ring around the oscillator

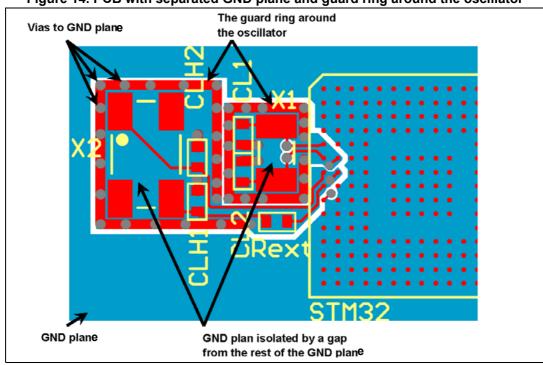

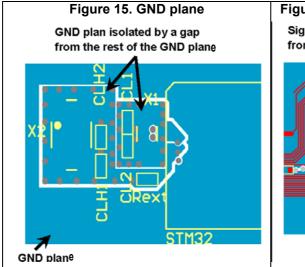

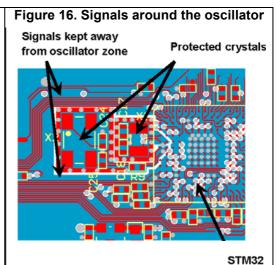

477


AN2867 Rev 16 47/59

#### Example 2

*Figure 17* is an example of a PCB that does not respect the guidelines provided in *Section 7.1*, for the following reasons:

- no ground planes around the oscillator component
- too long paths
- no symmetry between oscillator capacitances
- high crosstalk / coupling between paths
- too many test points.


Figure 17. Preliminary design (PCB design guidelines not respected)

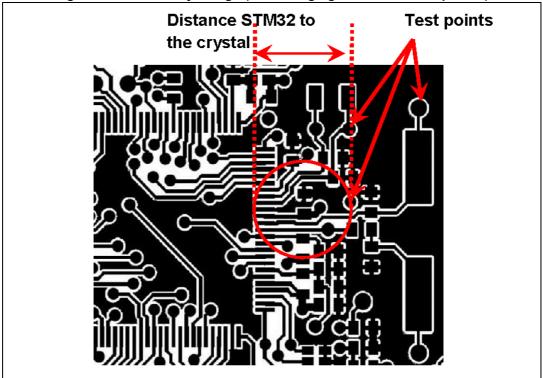



The PCB design has been improved according to the guidelines (see Figure 18):

- guard ring connected to the GND plane around the oscillator
- symmetry between oscillator capacitances
- · less test points
- no coupling between paths.

Figure 18. Final design (following guidelines)

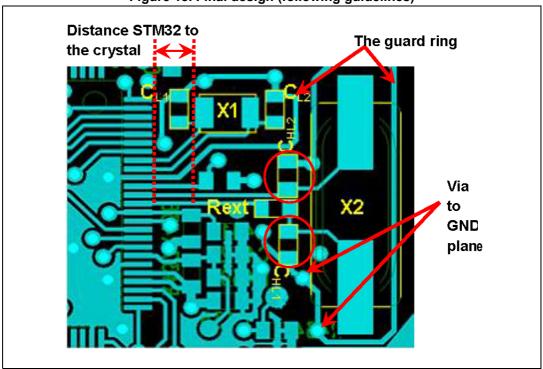

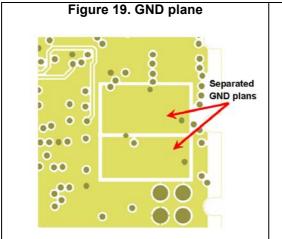

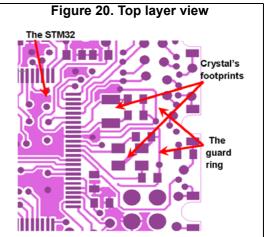

47/


AN2867 Rev 16 49/59

## Example 3

*Figure 21* is another example of PCB that does not respect the guidelines provided in *Section 7.1* (EMC tests likely to fail):

- no guard ring around oscillator components
- long paths.

Figure 21. PCB guidelines not respected

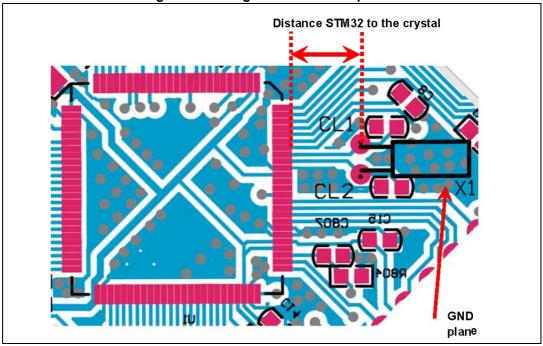

The layout has been improved to respect the guidelines (see *Figure 22*), EMC tests are likely to be passed:

- ground planes around the oscillator component
- short paths that link the STM32 to the oscillator
- symmetry between oscillator capacitances.

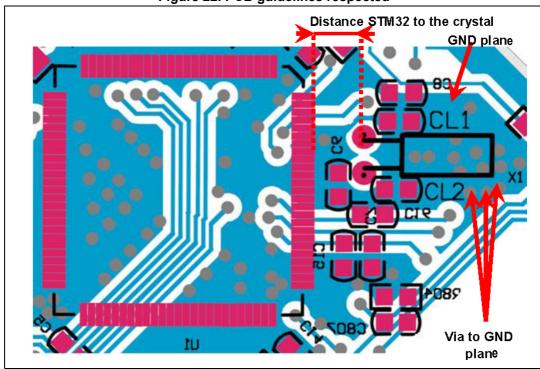


Figure 22. PCB guidelines respected

# 7.3 Soldering guidelines

In general, soldering is a sensitive process, especially for low-frequency crystals. To reduce the impact of such process on the crystal parameters user should consider that

- Exposing crystals to temperatures above their maximum ratings can damage the
  crystal and affect their ESR value. Refer to the crystal datasheet for the right reflow
  temperature curve (if not provided, ask the manufacturer).
- PCB cleaning is recommended to obtain the maximum performance by removing flux residuals from the board after assembly (even when using "no-clean" products in ultra-low-power applications).

# 7.4 LSE sensitivity to PC13 activity

The OSC32\_IN is sensitive to PC 13 activity, When PC13 is active (toggling) LSE clock may shift, depending upon the LSE drive configuration. For example, using PC\_13 as RTC\_OUT calibration for 512 Hz or 1 Hz it may disturb LSE oscillation loop, hence shift the calibration frequency.

4

AN2867 Rev 16 51/59

On products having the possibility to remap RTC\_OUT on another pin (for example PB2), it is recommended to use this remapping to avoid LSE disturbances.

AN2867 Reference documents

# 8 Reference documents

[1] E. Vittoz *High-Performance Crystal Oscillator Circuits: Theory and Application* IEEE Journal of solid State Circuits, Vol 23, No 3, June 1988 pp 774 - 783.



FAQs AN2867

#### 9 FAQs

#### Question

How can I know if my crystal is compatible with a given STM32 part?

#### **Answer**

Refer to Section 4: Guidelines to select a suitable crystal and external components.

#### Question

Can I use a 32.768 kHz crystal compatible with STM32 parts but not mentioned in Table 7?

#### **Answer**

Yes, you can. *Table 7* is not exhaustive, it is given as a reference for some selected crystal manufacturers, footprint size and crystal load capacitance.

#### Question

In my application, 32.768 kHz frequency very-low drift and high accuracy are mandatory to obtain an accurate clock without calibration. Which crystal load capacitance ( $C_L$ ) should I choose?

#### **Answer**

First, you must be sure that your crystal is compatible with the selected STM32 LSE. Then, it is highly recommended to use a crystal with low pullability, that is with  $C_L \ge 6$  pF:

- 7 pF is a good compromise between low drift and moderate power consumption
- 9 and 12.5 pF can be used in noisy environments, but impact the power consumption.

AN2867 Conclusion

#### 10 Conclusion

The most important parameter is the gain margin of the oscillator, which determines if the oscillator starts up or not. This parameter must be calculated at the beginning of the design phase, to choose the suitable crystal for the application. The second parameter is the value of the external load capacitors, to select in accordance with the  $C_L$  specification of the crystal (provided by the manufacturer). This determines the frequency accuracy of the crystal. The third parameter is the value of the external resistor used to limit the drive level. In the 32 kHz oscillator part, however, it is not recommended to use an external resistor.

Because of the number of variables involved, in the experimentation phase it is recommended to select components that have exactly the same properties as those that will be used in production, and operate with the same oscillator layout and in the same environment, to avoid unexpected behavior.

Recently, MEMS oscillators have emerged on the market. They are a good alternative to resonators-based oscillators, thanks to their reduced power consumption, small size (they do not require additional passive components such as external load capacitors), and cost. This kind of oscillator is compatible with all STM32 MCUs/MPUs, except for the STM32F1 and STM32L1 Series. When a MEMS oscillator is paired with an STM32 embedded oscillator, configure the latter in bypass mode.

AN2867 Rev 16 55/59

Revision history AN2867

# 11 Revision history

**Table 12. Document revision history** 

Date	Revision	Changes
20-Jan-2009	1	Initial release.
10-Nov-2009	2	DL formula corrected in Section 3.5.2: Another drive level measurement method.  Package column added to all tables in Section 6: Some recommended crystals for STM32 microcontrollers.  Recommended part numbers updated in Section 5.1: STM32-compatible high-speed resonators.
27-Apr-2010	3	Added Section 7: Some recommended crystals for STM8A/S microcontrollers.
25-Nov-2010	4	Updated Section 5.1: STM32-compatible high-speed resonators: removed Table 7: Recommendable condition (for consumer) and Table 8: Recommendable condition (for CAN bus); added Table 8: Recommendable conditions (for consumer); updated Murata resonator link.  Updated Section 5.1: STM32-compatible high-speed resonators: removed Table 13: EPSON TOYOCOM, Table 14: JFVNY®, and Table 15: KDS; Added Table 6: Recommendable crystals NEW LANDSCAPE TABLE.  Added Warning: after Figure 13.
30-Mar-2011	5	Section 5.1: STM32-compatible high-speed resonators: updated "STM32" with "STM8".  Table 16: Recommendable conditions (for consumer): replaced ceramic resonator part number "CSTSE16M0G55A-R0" by "CSTCE16M0V53-R0".
17-Jul-2012	6	Whole document restricted to STM32 devices.
19-Sep-2014	7	Changed STM32F1 into STM32 throughout the document. Added STM8AL Series in <i>Table 1: Applicable products</i> . Replace STM8 by STM32 in <i>Section :</i> and updated hyperlink. Added <i>Section 7: Tips for improving oscillator stability</i> . Remove section <i>Some PCB hints</i> .
19-Dec-2014	8	Updated Section 2: Oscillator theory.  Updated Section 3: Pierce oscillator design. Renamed section "Gain margin of the oscillator" into Section 3.4: Oscillator transconductance and content updated. Updated Section 3.6: Start-up time. Updated Section 3.7: Crystal pullability.  Updated Section 4: Guidelines to select a suitable crystal and external components.  Updated Section 5: Recommended resonators for STM32 MCUs/MPUs. Added Section 8: Reference documents.  Updated Section 10: Conclusion.

AN2867 Revision history

Table 12. Document revision history (continued)

Date	Revision	Changes
19-Feb-2015	9	Updated Section 2.3: Negative-resistance oscillator principles to specify the ratio between negative resistance and crystal ESR for STM8 and STM32 microcontrollers.  Added Section 3.8: Safety factor.  Added Check the Safety Factor of the oscillation loop step in Section 4.2: How to select an STM32-compatible crystal. Note moved from step 2 to 3 and updated.
		Renamed Table 7: Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products.
17-Aug-2015	10	Updated Figure 12: Classification of low-speed crystal resonators.  Added caution notes in Section 4.1: Low-speed oscillators embedded in STM32 MCUs / MPUs.  Added STM32F7, STM32F446xx, STM32F469/479xx and STM32L4 microcontrollers in Table 5: LSE oscillators embedded into STM32 MCUs/MPUs.
		Added STM32F411xx, STM32F446xx, STM32F469/479xx and STM32L4xx microcontrollers in <i>Table 6: HSE oscillators embedded in STM32 MCUs/MPUs</i> .
		Updated Table 7: Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products. Added Section 9: FAQs.
31-May-2017	11	Updated document title, Introduction, Section 9: FAQs, Section 10: Conclusion, title of Section 6: Recommended crystals for STM8AF/AL/S microcontrollers, and revision of text across the whole document.  Updated Table 5: LSE oscillators embedded into STM32 MCUs/MPUs, Table 6: HSE oscillators embedded in STM32 MCUs/MPUs and Table 7: Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products.  Updated caption of Table 8: KYOCERA compatible crystals (not exhaustive list), and added Table 9: NDK compatible crystals (not exhaustive list).  Updated Figure 12: Classification of low-speed crystal resonators.
21-Jan-2020	12	Updated document title, Section 2: Oscillator theory, Section 5.1: STM32-compatible high-speed resonators and Section 5.2: STM32-compatible low-speed resonators.  Updated Table 1: Applicable products, Table 5: LSE oscillators embedded into STM32 MCUs/MPUs, Table 6: HSE oscillators embedded in STM32 MCUs/MPUs, Table 7: Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products, Table 8: KYOCERA compatible crystals (not exhaustive list), Table 9: NDK compatible crystals (not exhaustive list), Table 10: Recommended conditions (for consumer) and Table 11: Recommended conditions (for CAN-BUS).  Minor text edits across the whole document.

Revision history AN2867

Table 12. Document revision history (continued)

Date	Revision	Changes
04-Dec-2020	13	Updated Table 7: Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products and its footnotes 2 and 3.  Updated footnotes of Table 5: LSE oscillators embedded into STM32 MCUs/MPUs.  Added Section 7.4: LSE sensitivity to PC13 activity.  Minor text edits across the whole document.
27-Jul-2021	14	Updated Section 2.2: Transconductance, Section 3.4: Oscillator transconductance, Section 4.2: How to select an STM32-compatible crystal and Section 5.1: STM32-compatible high-speed resonators Added Section 3.9: Oscillation modes and its subsections.  Updated Table 7: Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products.  Minor text edits across the whole document.
05-Oct-2021	15	Added notes in Section 3.5.2: Another drive level measurement method, Section 5.2: STM32-compatible low-speed resonators and Section 6.1: Part numbers of recommended crystal oscillators.  Added footnote 4 to Table 5: LSE oscillators embedded into STM32 MCUs/MPUs.  Updated Table 6: HSE oscillators embedded in STM32 MCUs/MPUs, Table 7: Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products and Table 9: NDK compatible crystals (not exhaustive list).  Minor text edits across the whole document.
22-Aug-2022	16	Updated Table 1: Applicable products, Table 5: LSE oscillators embedded into STM32 MCUs/MPUs, Table 7: Recommended crystal / MEMS resonators for the LSE oscillator in STM32 products, and Table 9: NDK compatible crystals (not exhaustive list). Updated Section 6.1: Part numbers of recommended crystal oscillators. Minor text edits across the whole document.

#### IMPORTANT NOTICE - PLEASE READ CAREFULLY

STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, enhancements, modifications, and improvements to ST products and/or to this document at any time without notice. Purchasers should obtain the latest relevant information on ST products before placing orders. ST products are sold pursuant to ST's terms and conditions of sale in place at the time of order acknowledgment.

Purchasers are solely responsible for the choice, selection, and use of ST products and ST assumes no liability for application assistance or the design of Purchasers' products.

No license, express or implied, to any intellectual property right is granted by ST herein.

Resale of ST products with provisions different from the information set forth herein shall void any warranty granted by ST for such product.

ST and the ST logo are trademarks of ST. For additional information about ST trademarks, please refer to <a href="https://www.st.com/trademarks">www.st.com/trademarks</a>. All other product or service names are the property of their respective owners.

Information in this document supersedes and replaces information previously supplied in any prior versions of this document.

© 2022 STMicroelectronics – All rights reserved



AN2867 Rev 16 59/59